

EE4306 Tutorial

Introduction to Microwave Office

This tutorial is an introduction in the use of Microwave Office, and is done in EL209 as a step by step learning exercise.

The task is to design and measure the frequency response of an audio crossover network using second order high pass and low pass networks. The loudspeakers are 8 ohm impedance and a crossover frequency of 3.5 kHz is required.

C. J. Kikkert
September 2004