

EE4306 Tutorial

Branchline Coupler

Calculate the impedances and line lengths required for a Branchline coupler with a coupled output 10 dB below the input signal (10% of the input power), so that 90% of the power is coupled to the main port.

C. J. Kikkert
September 2004