

EE4306 Tutorial

Helical Filter

Design a 4 resonator helical filter to have a centre frequency of 70 MHz, a bandwidth of 2 MHz, an insertion loss of less than 3 dB and input and output impedances of 50Ω . The filter is to occupy the smallest volume consistent with the insertion loss.

This was a question from the 2002 exam paper.

C. J. Kikkert

1 Nov 2005