

EE4306 VHDL Tutorial 5

Asynchronous Logic Toggle Flip-Flop

- 1 Draw the Logic Signal Flow Graph and the Excitation Matrix for a toggle Flip-Flop.
- 2 Obtain the required Boolean Algebra equations.
- 3 Write a VHDL module for this circuit
- 4 Test the operation of your module

C. J. Kikkert
18 August 2005